🛄 Mini-Circuits

Diminutive Impedance-Matching Splitters (AN-10-004)

Introduction

These tiny power splitters deliver full-sized performance transforming between 50 Ω and 75 Ω , from 5 to 1000 MHz.

Traditionally, power dividers/combiners are invaluable passive components that allow transmitters and receivers to combine or divide signals as necessary. Component availability for characteristic impedance of 50Ω is ample. A mixed impedance splitter (50Ω at input and 75Ω at output, or 75Ω at input and 50Ω at output) can help in certain signal processing applications, such as realization of 75Ω balanced amplifiers.

Basically, a power splitter is formed of an input impedance-matching section, a divider section, and a resistor. Consider a system that needs to split a signal from input at 50 Ω to two outputs at 75 Ω . As shown in Fig. 1, the impedance at the input of the divider is nominally 37.5 Ω . The matching transformer converts this impedance to 50 Ω input with minimal signal power loss. Oppositely, a system to split a signal from input at 75 Ω to output at 50 Ω is shown in Fig. 2. The impedance at the input of the divider is close to 25 Ω . The matching transformer converts this low impedance to 75 Ω at the RF input.

The resistor (R) plays a critical role in providing isolation between the two RF output ports. A capacitor is incorporated within the device to optimize frequency bandwidth.



Figure 1 – Input at 50Ω to Two Outputs at 75Ω



Figure 2– Input at 75Ω to Two Outputs at 50Ω

Construction

The base of Mini-Circuits matching splitter models SBTC-2-10-5075 and SBTC-2-10-7550 is constructed using Blue CellTM technology, which utilizes low temperature cofired ceramic (LTCC). This makes it possible to embed the resistor and part of the matching network within the power-splitter circuitry, while the base supports a ferrite transformer to form the divider and to complete the matching function. Connections between components are formed through the company's proprietary welding process. Please refer to application note AN-40-004 for reflow soldering guidance.

Performance

Model SBTC-2-10-5075 is a two-way splitter from 50Ω input to 75Ω output. It shows about 1dB insertion loss up to 860 MHz and 1.2dB at 1000 MHz (above the 3dB split); see Fig. 3. Also, it has excellent VSWR (Voltage Standing Wave Ratio) as shown in Fig. 4: 1.05 - 1.20 (typ.) at the input (Port S) and 1.15 - 1.35 (typ.) at the outputs (Ports 1 and 2) from 50 to 1000 MHz. The specifications are given in Table 1.

Model SBTC-2-10-7550 is a two-way splitter from 75Ω input to 50Ω output. It has less than 1dB insertion loss from 5 to 1000 MHz as Fig. 5 shows. VSWR is 1.25.(typ.) up to 600MHz at both input and output. It rises at higher frequencies; peaking at 1.40 (typ.) at the input. See Fig. 6. The specifications are in Table 2.

Both of these devices can handle input power level up to 0.5W when used as a splitter, and 0.125W when used as a power combiner.

FREQ. RANGE (MHz)	ISOLATION (dB)			INSERTION LOSS (dB) ABOVE 3.0 dB			PHASE UNBALANCE (Degrees)			AMPLITUDE UNBALANCE (dB)		
	L	М	U	L	M	U	L	M	U	L	Μ	U
f _∟ -f _∪	Typ. Min.	Typ. Min.	Typ. Min.	Typ. Max.	Typ. Max.	Typ. Max.	Max.	Max.	Max.	Max.	Max.	Max.
50-1000	25 16		20 15	0.7 1.2		1.0 1.6	3	_	5	0.6	—	0.5

Electrical Specifications

 $L = low range [f_{L} to 10 f_{L}] \qquad M = mid range [10 f_{L} to f_{U}/2] \qquad U = upper range [f_{U}/2 to f_{U}]$

Table 1 – Model SBTC-2-10-5075, 50 Ω Input to 75 Ω Output

FREQ. RANGE (MHz)	ISOLATION (dB)			INSERTION LOSS (dB) ABOVE 3.0 dB			PHASE UNBALANCE (Degrees)			AMPLITUDE UNBALANCE (dB)		
	L	М	U	L	М	U	L	Μ	U	L	Μ	U
f _L -f _U	Typ. Min.	Typ. Min.	Typ. Min.	Typ. Max.	Typ. Max.	Тур. Мах.	Max.	Max.	Max.	Max.	Max.	Max.
5-1000	23 13	24 20	26 20	0.5 1.3	0.6 1.1	0.7 1.5	6	3	5	0.8	0.5	0.5
L = low range [f, to 10 f,] M = mid range [10 f, to f,/2] U = upper range [f,/2 to f,]												

Electrical Specifications

Table 2 – Model SBTC-2-10-7550, 75Ω Input to 50Ω Output

SBTC-2-10-5075 INSERTION LOSS





SBTC-2-10-5075 VSWR

Figure 4



Figure 5



Figure 6

What are the applications for these products?

Example 1:

Usually, a cable system operates at 75Ω impedance. But, most of RF amplifiers have 50Ω impedance. By using the circuit shown below, Fig. 7, amplification of RF signals in a 75Ω system is possible with 50Ω amplifiers. With impedances matched in the circuit, maximum power will be transferred and the system designer has more choice of amplifiers.



Figure 7 – Balanced 50 Ω Amplifier in a 75 Ω System

Example 2:

Many RF communication systems are using cable network now, and therefore require wide-band 75 Ω RF switches. RF communication systems have traditionally been implemented in 50 Ω impedance; to match, switches are generally designed for 50 Ω . A pair of power splitters with 50 Ω input and 75 Ω output will enable a 50 Ω switch to be used in a 75 Ω cable network. Fig. 8 shows a circuit for selection of cable signals that can be used for network connection.



Figure 8 – Selecting 75 Ω Signals with a 50 Ω Switch

Conclusion

These newly developed products have diminutive size, small power loss and wide bandwidth. They combine two functions in one device – power splitting/combining and impedance matching, and have many practical applications.

© 2015 Mini-Circuits

information contained herein.

This document is provided as an accommodation to Mini-Circuits customers in connection with Mini-Circuits parts only. In that regard, this document is for informational and guideline purposes only. Mini-Circuits assumes no responsibility for errors or omissions in this document or for any

IMPORTANT NOTICE

Mini-Circuits may change this document or the Mini-Circuits parts referenced herein (collectively, the "Materials") from time to time, without notice. Mini-Circuits makes no commitment to update or correct any of the Materials, and Mini-Circuits shall have no responsibility whatsoever on account of any updates or corrections to the Materials or Mini-Circuits' failure to do so.

Mini-Circuits customers are solely responsible for the products, systems, and applications in which Mini-Circuits parts are incorporated or used. In that regard, customers are responsible for consulting with their own engineers and other appropriate professionals who are familiar with the specific products and systems into which Mini-Circuits' parts are to be incorporated or used so that the proper selection, installation/integration, use and safeguards are made. Accordingly, Mini-Circuits assumes no liability therefor.

In addition, your use of this document and the information contained herein is subject to Mini-Circuits' standard terms of use, which are available at Mini-Circuits' website at www.minicircuits.com/homepage/terms_of_use.html.

Mini-Circuits and the Mini-Circuits logo are registered trademarks of Scientific Components Corporation d/b/a Mini-Circuits. All other third-party trademarks are the property of their respective owners. A reference to any third-party trademark does not constitute or imply any endorsement, affiliation, sponsorship, or recommendation: (i) by Mini-Circuits of such third-party's products, services, processes, or other information; or (ii) by any such third-party of Mini-Circuits or its products, services, processes, or other information.