

AN-30-001

**Application Note on** 

## DO IT YOURSELF LOW-COST DIRECTIONAL COUPLERS

Radha Setty Weiping Zheng

Mini-Circuits Engineering Department, P.O. Box 350166, Brooklyn, NY 11235

# Do it yourself low-cost Directional Couplers

#### **Engineering Department**

Mini-Circuits, Brooklyn, NY 11235

#### Introduction:

Ever expanding applications of RF and Microwaves for Wireless and Cable applications have revived the development efforts of components at these frequencies. There is a continuing demand to reduce the cost and increase the performance and quality at the same time. Mini-Circuits is working to satisfy these goals and has introduced a new Directional Couplers series to satisfy the demands of the market. These couplers are designed to need only commercially available low-cost off-the-shelf chip resistors as external components, and are designed for automated manufacturing to achieve low overall cost.

What Constitutes a Directional Coupler :

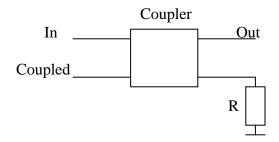


Fig.1 Block Schematic of a Directional Coupler

**Fig 1** is the block schematic of a Directional Coupler. The heart of the coupler is supplied by Mini Circuits as a component. When used with one external chip component a resistor R a complete coupler is realized. Mini-Circuits has released a series of couplers for both 50 and 75 ohm operation. These couplers have prefix "TCD" in their model number.

### Construction of the "TCD" device

TCD-series couplers use one ferromagnetic core transmission line transformer to realize a directional coupler. The base of the device is made of plastic with embedded leads, which makes the construction very rugged. The leads are solder plated for excellent solderability. All connections from the transformers to the header are made by welding. This helps to ensure preciseness of the assembly, with resulting high performance repeatability, as well as preventing any disconnection during reflow.

### Performance of the Coupler

Mini-Circuits has introduced 9 couplers, covering the frequency range of 5 to 1000 MHz. TCD-13-4 is designed for 50 ohm and TCD-13-4-75 is a 13 dB coupler for 75 ohm characteristic impedance. **Fig 2** is a photograph of the coupler and **Table I** gives the specifications. Also shown in Table I are the specifications for couplers of other coupling values. **Fig 3** shows the insertion loss of TCD-13-4-75. The insertion loss of the coupler is typically 0.9 dB over the band. **Fig 4** shows the directivity vs. frequency, which is typically 15 dB over the band. **Fig 5** shows the coupling vs. frequency, which is typically 20 dB (VSWR, 1.22:1). Circuit board layout plays an important part in the performance of the coupler. In order to minimize parasitic effects, the suggested layout shown in **Fig 7** should be used. This series needs only an external resistor of 0805 size. The chip resistor should have a nominal value of 75 or 50 ohms for TCD-13-4-75 and TCD-13-4 respectively. Actual data of other couplers shown in table I can be viewed instantly at http://www.minicircuits.com

#### Conclusion

Nine couplers have been introduced to operate over 5-1000 MHz. Due to all-welded connections the couplers are very rugged. The product has been designed to be manufactured in automated set-ups which helps lower the cost. Further cost reduction is obtained by designing the unit to work with a low-cost off-the-shelf chip resistor used as external component. These units are designed for automated pick and place manufacturing.

Table I ELECTRICAL SPECIFICATIONS																			
MODEL NO.	FREQ. RANGE (MHz)	COUP (d)	MAINLINE LOSS (dB)						DIRECTIVITY (dB)						VSWR (:1)	POWER INPUT, W		RESIS- TOR (Ω)	
		Max.		L		Μ			U		L		М		U				
		Nom.	Flatness	Typ.	Max.	Typ.	Max.	Typ.	Max.	Тур.	Min.	Typ.	Min.	Typ.	Min.	Тур	L Max.	MU Max.	
TCD-9-1W	5-750	8.9±0.5	±0.5	1.2	2.1	1.2	1.8	1.5	1.9	21	17	17	10	15	-	1.30	0.5	1	50
TCD-9-1W-75	5-500	8.9±0.5	±0.5	1.3	2.1	1.2	1.8	1.3	1.9	21	17	17	10	12	-	1.30	0.5	1	75
TCD-10-1W	10-750	10.3±0.5	±0.8	1.3	2.1	1.2	1.6	1.4	2.0	22	17	18	14	15	-	1.30	0.5	1	50
TCD-10-1W-75	10-750	10.5±0.5	±0.7	1.6	2.1	1.4	1.9	1.5	2.0	22	17	18	14	14	-	1.30	0.5	1	75
TCD-13-4	5-1000	13.0±0.5	±0.6	0.7	1.3	0.7	1.3	0.8	1.5	21	17	18	12	15	-	1.20	0.5	1	50
TCD-13-4-75	5-1000	13.0±0.5	±0.9	1.0	1.8	0.8	1.3	1.1	1.5	22	17	15	-	12	-	1.20	0.5	1	75
TCD-18-4	5-1000	17.9±0.5	±0.6	0.7	1.3	0.7	1.1	1.0	1.4	22	11	20	15	18	-	1.20	1	1	50
TCD-18-4-75	10-1000	18.0±0.5	±0.9	0.9	1.3	0.7	1.2	0.8	1.3	20	15	22	15	18	-	1.20	1	1	75
TCD-20-4	5-1000	20.0±0.5	±0.8	0.3	0.9	0.4	0.8	0.7	1.1	20	11	21	15	15	-	1.20	1	1	50


 $\mathbf{L} = \text{low range} [f_{L} \text{ to } 10 f_{L}]$ 

 $\mathbf{M} = mid \ range \ [10 \ f_L \ to \ f_U/2] \qquad \mathbf{U} = upper \ range \ [f_U/2 \ to \ f_U]$ 


Price: \$5.95 (Qty.10-19)




Fig. 2

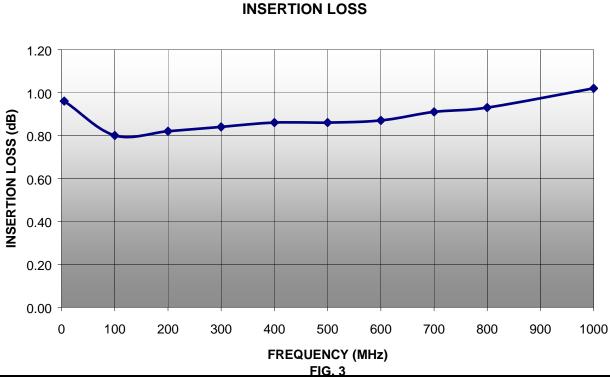

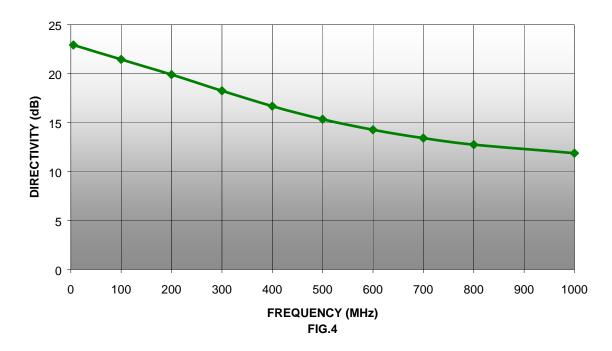
TCD-13-4-75 INSERTION LOSS TCD-13-4-75 DIRECTIVITY



TCD-13-4-75 COUPLING

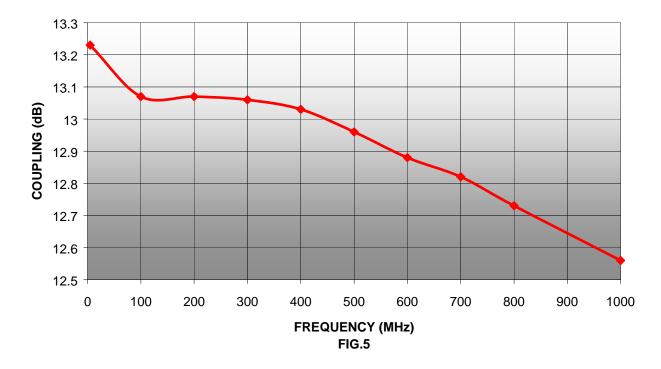

TCD-13-4-75 RETURN LOSS

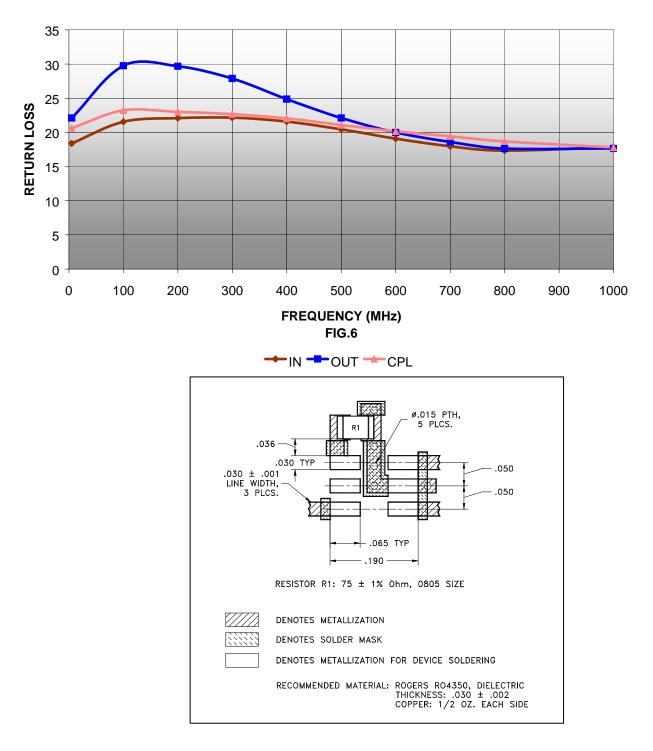

**FIG. 7** 

#### © 2015 Mini-Circuits

#### IMPORTANT NOTICE

This document is provided as an accommodation to Mini-Circuits customers in connection with Mini-Circuits parts only. In that regard, this document is for informational and guideline purposes only. Mini-Circuits assumes no responsibility for errors or omissions in this document or for any information contained herein.

Mini-Circuits may change this document or the Mini-Circuits parts referenced herein (collectively, the "Materials") from time to time, without notice. Mini-Circuits makes no commitment to update or correct any of the Materials, and Mini-Circuits shall have no responsibility whatsoever on account of any updates or corrections to the Materials or Mini-Circuits' failure to do so.

Mini-Circuits customers are solely responsible for the products, systems, and applications in which Mini-Circuits parts are incorporated or used. In that regard, customers are responsible for consulting with their own engineers and other appropriate professionals who are familiar with the specific products and systems into which Mini-Circuits' parts are to be incorporated or used so that the proper selection, installation/integration, use and safeguards are made. Accordingly, Mini-Circuits assumes no liability therefor.

In addition, your use of this document and the information contained herein is subject to Mini-Circuits' standard terms of use, which are available at Mini-Circuits' website at www.minicircuits.com/homepage/terms\_of\_use.html.

Mini-Circuits and the Mini-Circuits logo are registered trademarks of Scientific Components Corporation d/b/a Mini-Circuits. All other third-party trademarks are the property of their respective owners. A reference to any third-party trademark does not constitute or imply any endorsement, affiliation, sponsorship, or recommendation: (i) by Mini-Circuits of such third-party's products, services, processes, or other information; or (ii) by any such third-party of Mini-Circuits or its products, services, processes, or other information.