

Ultra-Wideband, Low-Loss Couplers for Cable TV and Broadband Access Systems (DOCSIS® 3.1)

I. BACKGROUND

This application note discusses the use of ultra-low loss, broadband distributed couplers in 75Ω systems such as broadband services over cable television networks (CATV).

CATV systems require continuous monitoring of output power in the forward (downstream) path throughout the network to ensure consistent signal transmission. This is often achieved by using a low-loss coupler at the output of a power amplifier and adjusting the gain to compensate for any variations in power.

The DOCSIS 3.1 standard specifies a downstream bandwidth from 40 to 1220 MHz. Bandwidth this wide, roughly 30:1, generally necessitates the use of core and wire couplers to achieve the required coupling flatness vs. frequency, and to accurately sample signal power over the full band. While core and wire coupler designs easily cover the required frequency range with excellent flatness, they tend to be lossy, typically sacrificing 1 dB of power or greater. This results in the need for additional power amplifiers or a higher compression amplifier in the transmit path to compensate for those losses, increasing system cost, power dissipation, and component count.

II. STRIPLINE SOLUTION

Distributed couplers utilizing stripline construction provide outstanding insertion loss and return loss by comparison to core and wire designs. The tradeoff is that they don't provide flat coupling over the required bandwidth. Figures 1a and 1b below show comparisons of core and wire model, ADC-17-122-75+ with a new stripline model, BDCH-122-75+. Note that the stripline coupler achieves superior mainline loss while the core and wire design achieves superior coupling flatness across the band.

While stripline couplers may not provide flat coupling, they do provide excellent repeatability of performance, giving us predictable coupling values at a given frequency. This makes it possible to compensate for frequency-dependent variations in coupling by adding a fixed equalizer on the coupling line. This approach is described in detail below using model BDCH-122-75+.

Mini-Circuits' BDCH-122-75+ stripline-based coupler has a frequency range from 40 to 1250 MHz with 2W RF input power handling, just 0.15 dB mainline loss and 25 dB typical return loss. While its coupling response varies over frequency, its high-quality stripline construction ensures that those variations are highly repeatable, and the methods discussed below may be used to design BDCH-122-75+ into DOCSIS 3.1 systems and exploit the low insertion loss of the stripline design.

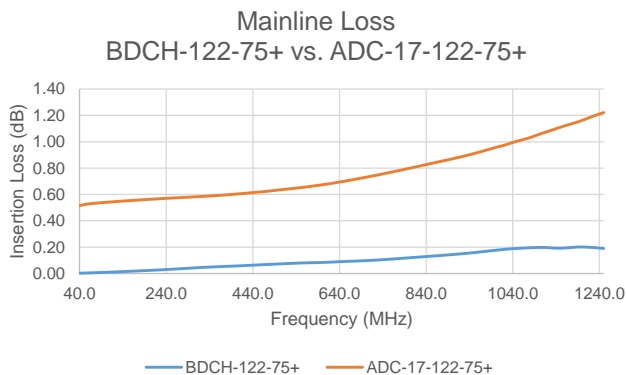


Figure 1a: Comparison of mainline loss between stripline coupler BDCH-122-75+ and core and wire coupler ADC-17-122-75+.

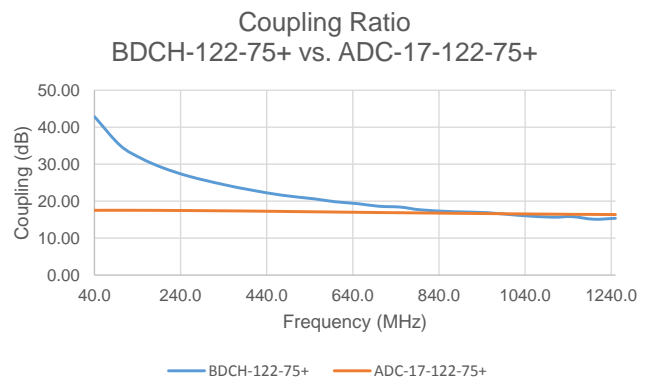


Figure 1b: Comparison of coupling flatness between stripline coupler BDCH-122-75+ and core and wire coupler ADC-17-122-75+.

III. FLATTENING COUPLING ATTENUATION WITH A FIXED EQUALIZER

Figure 2 shows a functional schematic of BDCH-122-75+ on a transmission line with an equalizer on the coupling line to compensate for the variations in coupling attenuation. The equalizer's attenuation will increase over frequency as coupling attenuation decreases. When combined in series on the coupling line as shown in the configuration below, the equalizer will produce flat coupling attenuation over the entire 40

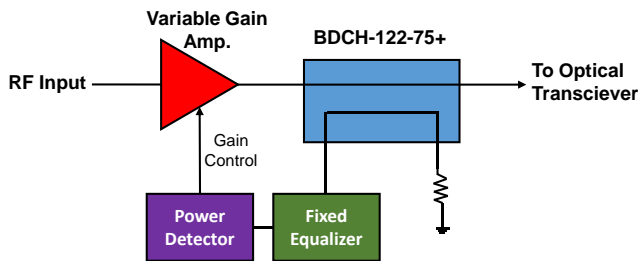


Figure 2: Functional schematic of stripline coupler in transmission path with a fixed equalizer on the coupled line.

to 1250 MHz band.

As proof of concept, Mini-Circuits developed a custom fixed equalizer to pair with BDCH-122-75+. As shown in the measurement plot in figure 3, with a well-designed equalizer, BDCH-122-75+ can achieve coupling flatness of better than ± 1 dB over the full DOCSIS 3.1 downstream band. The result is an extremely low-loss coupler for broadband 75 Ω systems with 44 dB nominal coupling.

IV. CONCLUSION

Using conventional coupler approaches, monitoring forward path output power from the head-end and network nodes in DOCSIS 3.1 systems would require a tradeoff of thru power in order to achieve the necessary coupling flatness for accurate power sampling and gain control. However, by exploiting the predictable variation in coupling attenuation of Mini-Circuits' stripline coupler, BDCH-122-75+, customers can use a fixed equalizer to achieve flat coupling over the full downstream band while also benefitting from the low insertion loss and excellent return loss of the stripline coupler design. This approach provides an ideal solution for power monitoring in CATV and broadband access systems conforming to the DOCSIS

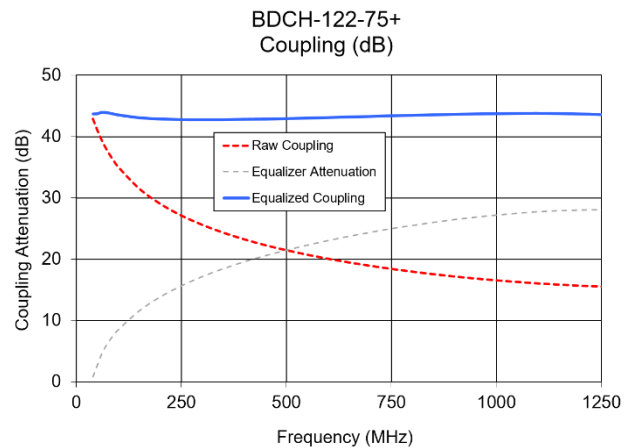


Figure 3: measurement plot of coupling attenuation for BDCH-122-75+ with fixed equalizer on the coupled line. 3.1 standard.

The technique illustrated in this article may also be used in other applications that require both flat coupling and outstanding signal power transmission across wide bandwidths. Mini-Circuits offers a selection of distributed, stripline coupler models for 50 Ω and 75 Ω circuits spanning 50 MHz to 6 GHz. For custom fixed equalizer designs for your board, please contact apps@minicircuits.com or your authorized Mini-Circuits sales representative.

IMPORTANT NOTICE

© 2017 Mini-Circuits

This document is provided as an accommodation to Mini-Circuits customers in connection with Mini-Circuits parts only. In that regard, this document is for informational and guideline purposes only. Mini-Circuits assumes no responsibility for errors or omissions in this document or for any information contained herein.

Mini-Circuits may change this document or the Mini-Circuits parts referenced herein (collectively, the "Materials") from time to time, without notice. Mini-Circuits makes no commitment to update or correct any of the Materials, and Mini-Circuits shall have no responsibility whatsoever on account of any updates or corrections to the Materials or Mini-Circuits' failure to do so.

Mini-Circuits customers are solely responsible for the products, systems, and applications in which Mini-Circuits parts are incorporated or used. In that regard, customers are responsible for consulting with their own engineers and other appropriate professionals who are familiar with the specific products and systems into which Mini-Circuits' parts are to be incorporated or used so that the proper selection, installation/integration, use and safeguards are made. Accordingly, Mini-Circuits assumes no liability therefore.

In addition, your use of this document and the information contained herein is subject to Mini-Circuits' standard terms of use, which are available at Mini-Circuits' website at www.minicircuits.com/homepage/terms_of_use.html.

Mini-Circuits and the Mini-Circuits logo are registered trademarks of Scientific Components Corporation d/b/a Mini-Circuits. All other third-party trademarks are the property of their respective owners. A reference to any third-party trademark does not constitute or imply any endorsement, affiliation, sponsorship, or recommendation: (i) by Mini-Circuits of such third-party's products, services, processes, or other information; or (ii) by any such third-party of Mini-Circuits or its products, services, processes, or other information.